


GENERAL APTITUDE

Q. No. 1 - 5 Carry One Mark Each

1.	She h	as a sharp tongue and it can occasionally turn							
	(A)	hurtful	(B)	left		(C)	methodical	(D)	vital
Answ	er:	(A)							
2.	Some	table are shelves.	Some	shel	ves are c	hairs. All	chairs are benche	s. Whi	ch of the following
	concl	usion can be deduce	ed fron	n the j	preceding	sentences	?		
	(i)	At least one bench	is a ta	ble					
	(ii)	At least one shelf i	is a bei	nch					
	(iii)	At least one chair	is a tab	ole					
	(iv)	All benches are ch	airs						
	(A)	only (i)	(B)	only	(ii)	(C)	only (ii) and (iii)	(D)	only (iv)
Answ	er:	(B)							
3.	40%	of deaths on city re	oads n	nay be	attribute	ed to drunl	ken driving. The n	umber	of degree needed to
	repres	sent this as a slice o	f a pie	chart	is				
	(A)	120	(B)	144		(C)	160	(D)	212
Answ		(B)							
4.	In the	e summer, water con	nsump	tion is	known t	o decrease	overall by 25%. A	water	Board official states
	that i	nat in the summer household consumption decreases by 20%, while other consumption increases by							
	70%.	ı.							
	Whic	ch of the following statement is correct?							
	(A)	The ratio of household to other consumption is 8/17							
	(B)	The ratio of household to other consumption is 1/17							
	(C)	The ratio of household to other consumption is 17/8							
	(D)	There are errors in the official's statement							
Answ	er:	(D)							



5.	I	made arrang	ement	s had I	· -	informe	ed earlier.		
	(A)	could have, been				(B)	would have	, being	
	(C)	had, have				(D)	had been, b	een	
Ansv	ver:	(A)							
			Q	. No. 6	6- 10 Car	ry Two M	Iarks Each		
6.	"If yo	ou are looking for a	histor	y of Ir	ndia, or fo	or an accou	unt of the rise	and fall of the	he British Raj, or for
	the re	eason of the cleavin	g of tl	ne sub	continent	into two i	nutually anta	gonistic part	s and the effects this
	mutil	ation will have in	the re	spectiv	ve section	n, and ulti	mately on A	sia, you will	not find it in these
	pages	s; for though I have	spent	a lifeti	ime in the	e country.	I lived too ne	ar the seat of	f events, and was too
	intim	ately associated wi	th the	actors,	to get th	e perspect	ive needed fo	r the imparti	al recording of these
	matte	ers".							
	Here	, the word 'antagon	istic' i	s close	est in mea	ning to			
	(A)	impartial	(B)	argui	mentative	(C)	separated	(D)	hostile
Ansv	ver:	(D)							
7.	There	e are 3 Indians and	3 Chii	nese in	a group	of 6 peopl	le. How many	y subgroups	of this group can we
	choo	se so that every sub	group	has at	least one	Indian?			
	(A)	56	(B)	52		(C)	48	(D)	44
Ansv	ver:	(A)							
8.	A co	ntour line joints lo	cations	havir	ng the sar	ne height	above the mo	ean sea level	I. The following is a
		our plot of a geograp			_				_

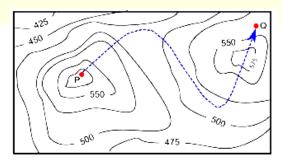



The path from P	to Q is best desc	ribed by
-----------------	-------------------	----------

- (A) Up-Down-Up-Down
- (B) Down-Up-Down-Up
- (C) Down-Up-Down
- (D) Up-Down-Up

Answer: (C)

- 9. Trucks (10m long) and cars (5 m long) go on a single lane bridge. There must be a gap of atleast 20 m after each truck and a gap of atleast 15m after each car. Trucks and cars travel at a speed of 36 km/h. If cars and trucks go alternatively, what is the maximum number of vehicles that can use the bridge in one hour?
 - (A) 1440
- (B) 1200
- (C) 720
- (D) 600

Answer: (A)

- 10. S, T, U, V, W, X, Y and Z are seated around a circular table. T's neighbours are Y and V. Z is seated third to the left of T and second to the right of S.U'sneighbours are S and Y; and T and W are not seated opposite each other. Who is third to the left of V?
 - (A) X
- (B) W
- (C) U
- (D) T

Answer:

(A)



ELECTRONICS AND COMMUNICATION ENGINEERING

Q. No. 1 to 25 Carry One Mark Each

1.	The clock frequency of an 8085 microprocessor is 5 MHz. If the time required to execute an
	instruction is 1.4 µs, then the number of T-states needed for executing the instruction is

- (A) 1
- (B) 6
- (C) 7
- (D) 8

Answer: (C)

2. Consider a single input single output discrete-time system with x[n] as input and y[n] as output, where the two are related as

$$y[n] = \begin{cases} n |x[n]| & \text{for } 0 \le n \le 10 \\ x[n] - x[n-1] & \text{otherwise} \end{cases}$$

Which one of the following statements is true about the system?

(A) It is causal and stable

(B) It is causal but not stable

(C) It is not causal but stable

(D) It is neither causal nor stable

Answer: (A)

3. Consider the following statement about the linear dependence of the real valued functions $y_1 = 1$, $y_2 = x$ and $y_3 = x^2$, over the field of real numbers.

I. y_1, y_2 and y_3 are linearly independent on $-1 \le x \le 0$

II. y_1, y_2 and y_3 are linearly dependent on $0 \le x \le 1$

III. y_1, y_2 and y_3 are linearly independent on $0 \le x \le 1$

IV. y_1, y_2 and y_3 are linearly dependent on $-1 \le x \le 0$

Which one among the following is correct?

(A) Both I and II are true

(B) Both I and III are true

(C) Both II and IV are true

(D) Both III and IV are true

Answer: (B)



4. Consider the 5×5 matrix

$$A = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ 5 & 1 & 2 & 3 & 4 \\ 4 & 5 & 1 & 2 & 3 \\ 3 & 4 & 5 & 1 & 2 \\ 2 & 3 & 4 & 5 & 1 \end{bmatrix}$$

It is given that A has only one real eigen value. Then the real eigen value of A is

- (A) -2.5
- (B) 0
- (C) 15
- (D) 25

Answer: (C)

Click here to watch video explanation

The voltage of an electromagnetic wave propagating in a coaxial cable with uniform characteristic impedance is $V(\ell) = e^{-\gamma \ell + j\omega t}$ volts, where ℓ is the distance along the length of the cable in meters. $\gamma = (0.1 + j40)m^{-1} \text{ is the complex propagation constant, and } \omega = 2\pi \times 10^9 \, \text{rad/s} \text{ is the angular frequency.Theabsolute value of the attenuation in the cable in dB/meter is ______.}$

Answer:

(0.868)

Click here to watch video explanation


- 6. A bar of Gallium Arsenide (GaAs) is doped with Silicon such that the Silicon atoms occupy Gallium and Arsenic sites in the GaAs crystal. Which one of the following statement is true?
 - (A) Silicon atoms act as p-type dopants in Arsenic sites and n-type dopants in Gallium sites
 - (B) Silicon atoms act as n-type dopants in Arsenic sites and p-type dopants in Gallium sites
 - (C) Silicon atoms act as p-type dopants in Arsenic as well as Gallium sites
 - (D) Silicon atoms act as n-type dopants in Arsenic as well as Gallium sites

Answer: (A)

- 7. The rank of the matrix $M = \begin{bmatrix} 5 & 10 & 10 \\ 1 & 0 & 2 \\ 3 & 6 & 6 \end{bmatrix}$ is
 - (A) 0
- (B) 1
- (C) 2
- (D) 3

Answer: (C)

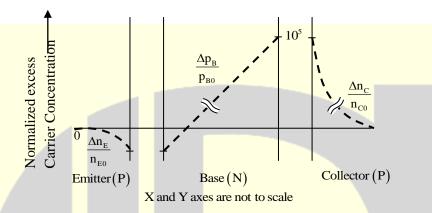8. For a narrow base PNP BJT, the excess minority carrier concentration (Δn_E for emitter, Δp_B for base. Δn_C for collector) normalized to equilibrium minority carrier concentration (n_{E0} for emitter, p_{B0} for base, n_{C0} for collector) in the quasi-neutral emitter, base and collector regions are shown below. Which one of the following biasing modes is the transistor operating in?



- (A) Forward active
- (B) Saturation
- (C) Inverse active
- (D) Cutoff


Answer: (C)

Click here to watch video explanation

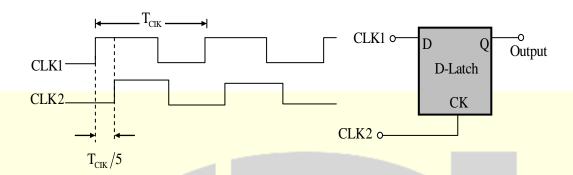- **9.** The Miller effect in the context of a Common Emitter amplifier explains
 - (A) an increase in the low-frequency cutoff frequency
 - (B) an increase in the high-frequency cutoff frequency
 - (C) a decrease in the low-frequency cutoff frequency
 - (D) a decrease in the high-frequency cutoff frequency

Answer: (D)

Consider the D-Latch shown in the figure, which is transparent when its clock input CK is high and **10.** has zero propagation delay.




In the figure, the clock signal CLK1 has a 50% duty cycle and CLK2 is a one-fifth period delayed version of CLK1.


The duty cycle at the output latch in percentage is ______.


(30) Answer:


Which of the following can be pole-zero configuration of a phase-lag controller (lag compensator)? 11.

(B)

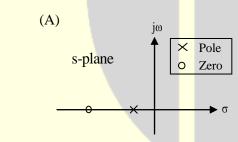

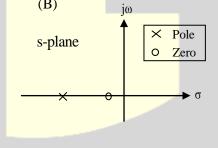

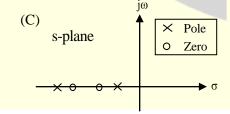


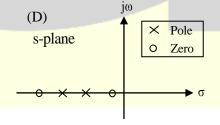


Answer: (A)



 
12. In the latch circuit shown, the NAND gates have non-zero, but unequal propagation delays. The present input condition is: P = Q = 0. If the input condition is changed simultaneously to P = Q = 1, the outputs X and Y are




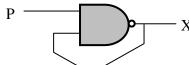


(B) either X = '1', Y = '0' or X = '0', Y = '1'

 (C) either
$$X = '1'$$
, $Y = '1'$ or $X = '0'$, $Y = '0'$



 

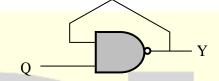

Answer: (B)

13. Three fair cubical dice are thrown simultaneously. The probability that all three dice have the same number of dots on the faces showing up is (up to third decimal place) _____.

Answer: (0.028)

Click here to watch video explanation

14. A periodic signal x(t) has a trigonometric Fourier series expansion

$$x(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t).$$

If $x(t) = -x - (t) = -x(t - \pi/\omega_0)$, we can conclude that


- (A) a_n are zero for all n and b_n are zero for n even
- (B) a_n are zero for all n and b_n are zero for n odd
- (C) a_n are zero for n even and b_n are zero for n odd
- (D) a_n are zero for n odd and b_n are zero for n even

Answer: (A)



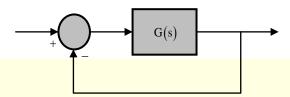15. The open loop transfer function $G(s) = \frac{(s+1)}{s^p(s+2)(s+3)}$

Where p is an integer, is connected in unity feedback configuration as shown in figure.



Given that the steady state error is zero for unit step input and is 6 for unit ramp input, the value of the parameter p is _____.


Answer: (1)

- 16. An $n^+ n$ Silicon device is fabricated with uniform and non-degenerate donor doping concentrations of $N_{D1} = 1 \times 10^{18} \, \text{cm}^{-3}$ and $N_{D2} = 1 \times 10^{15} \, \text{cm}^{-3}$ corresponding to the n^+ and n regions respectively. At the operational temperature T, assume complete impurity ionization, $kT/q = 25 \, \text{mV}$, and intrinsic carrier concentration to be $n_i = 1 \times 10^{10} \, \text{cm}^{-3}$. What is the magnitude of the built-in potential of this device?
 - (A) 0.748V
- (B) 0.460V
- (C) 0.288V
- (D) 0.173V

Answer: (D)

Click here to watch video explanation

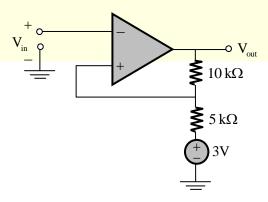17. For the operational amplifier circuit shown, the output saturation voltages are ± 15 V. The upper and lower threshold voltages for the circuit are, respectively.



(A) +5V and -5V

(B) +7V and -3V


(C) +3V and -7V

(D) +3V and -3V

Answer: (B

Click here to watch video explanation

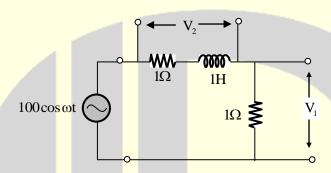
18. In the circuit shown, the positive angular frequency ω (in radians per second) at which magnitude of the phase difference between the voltages V_1 and V_2 equals $\frac{\pi}{4}$ radians, is _____.





Answer: (1)


Click here to watch video explanation

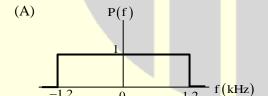19. In a digital communication system, the overall pulse shape p(t) at the receiver before the sampler has the Fourier transform P(f). If the symbols are transmitted at the rate of 2000 symbols per second, for which of the following cases is inter symbol interference zero?



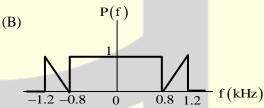

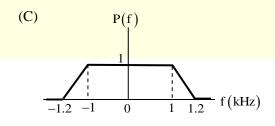

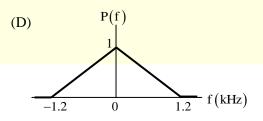

Answer: (B)



20. Consider a stable system with transfer function

$$G(s) = \frac{s^{p} + b_{1}s^{p-1} + \dots + b_{p}}{s^{q} + a_{1}s^{q-1} + \dots + a_{q}}$$

Where b_1, \dots, b_p and $a_1, \dots a_q$ are real valued constants. The slope of the Bode log magnitude curve of G(s) converges to $-60 \, dB/decade$ as $\omega \to \infty$. A possible pair of values for p and q is

(A) p = 0 and q = 3

(B) p = 1 and q = 7

(C) p = 2 and q = 3

(D) p = 3 and q = 5

Answer: (A)

- 21. A good transconductance amplifier should have
 - (A) high input resistance and low output resistance
 - (B) low input resistance and high output resistance
 - (C) high input and output resistances
 - (D) low input and output resistance

Answer: (C)

Click here to watch video explanation

22. Let (X_1, X_2) be independent random variables. X_1 has mean 0 and variance 1, while X_2 has mean 1 and variance 4. The mutual information $I(X_1; X_2)$ between X_1 and X_2 in bits is ______.

Answer: (0)

- 23. Consider the following statements for continuous-time linear time invariant (LTI) systems.
 - There is no bounded input bounded output (BIBO) stable system with a pole in the right half of the complex plane.
 - **II.** There is no causal and BIBO stable system with a pole in the right half of the complex plane. Which one among the following is correct?

	(A)	Both I and II are true	(B)	Both I and II are not true		
	(C)	Only I is true	(D)	Only II is true		
Answ	ver:	(D)				
24.	Whic	h one of the following statements about differ	ential pul	se code modulation (DPCM) is true?		
	(A)	The sum of message signal sample with it	ts predict	ion is quantized		
	(B)	The message signal sample is directly qua	antized, a	and its prediction is not used		
	(C)	The difference of message signal sample	and a ran	dom signal is quantized		
	(D)	The difference of message signal sample	with its p	oredictions is quantized		
Answ	ver:	(D)		Click here to watch video explanation		
25.	Cons	ider a wireless communication link between	een a trai	nsmitter and a receiver located in free space,		
	with	finite and strictly positive capacity. If the	ne effecti	ive areas of the transmitter and the receiver		
	anten	nas, and the distance between them are al	l doubled	l, and everything else remains unchanged, the		
	maxi	mum capacity of the wireless link				
	(A)	increases by a factor of 2	(B)	decrease by a factor 2		
	(C)	remains unchanged	(D)	decreases by a factor of $\sqrt{2}$		
Answ	ver:	(C)				
		Q. No. 26 to 55 Car	ry Two l	Marks Each		
		`\				
26.	Starti	x = 1, the solution of the equation	$n x^3 + x =$	=1, after two iterations of Newton-Raphson's		
	method (upto two decimal places) is					
Answ	ver:	(0.69)		Click here to watch video explanation		
27.	In bir	nary frequency shift keying (FSK), the give	en signal	waveform are		

 $u_0(t) = 5\cos(20000\pi t); 0 \le t \le T$, and

 $u_1(t) = 5\cos(22000\pi t); 0 \le t \le T,$



Where T is the bit-duration interval and t is in seconds. Both $u_0(t)$ and $u_1(t)$ are zero outside the interval $0 \le t \le T$. With a matched filter (correlator) based receiver, the smallest positive value of T (in milliseconds) required to have $u_0(t)$ and $u_1(t)$ uncorrelated is


- (A) 0.25ms
- (B) 0.5ms
- (C) 0.75ms
- (D) 1.0ms

Answer:

(B)

Click here to watch video explanation

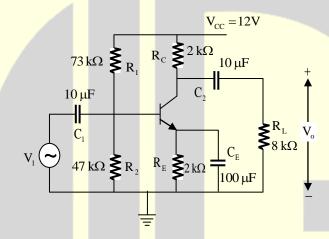28. For the DC analysis of the Common-Emitter amplifier shown, neglect the base current and assume that the emitter and collector current are equal.



Given that $V_T = 25 \text{mV}$, $V_{BE} = 0.7 \text{V}$, and the BJT output resistance r_0 is practically infinite. Under these conditions, the midband voltage gain magnitude $A_V = \left| V_o / V_i \right| V / V$, is ______.

Answer: (128)

Click here to watch video explanation

29. The figure shows an RLC circuit exited by the sinusoidal voltage $100\cos(3t)$ volts, where t is in seconds.

The ratio $\frac{\text{amplitude of } V_2}{\text{amplitude of } V_1}$ is _____.

seconds. V_1 4Ω 1H 5Ω V_2 $\frac{1}{36}F$

Answer: (2.6)

GATEFORUM Engineering C

Which one of the following is the general solution of the first order differential equation **30.**

 $\frac{dy}{dx} = (x + y - 1)^2$, where x, y are real?

(A) $y = 1 + x + \tan^{-1}(x + c)$, where c is a constant

(B) $y = 1 + x + \tan(x + c)$, where c is a constant

- (C) $y = 1 x + \tan^{-1}(x + c)$, where c is a constant
- (D) $y = 1 - x + \tan(x + c),$ where c is a constant

(D) Answer:

Click here to watch video explanation

31. A linear time invariant (LTI) system with the transfer function

$$G(s) = \frac{k(s^2 + 2s + 2)}{(s^2 - 3s + 2)}$$

is connected in unity feedback configuration as shown in the figure.



For the closed loop system shown, the root locus for $0 < k < \infty$ intersects the imaginary axis for $k = \infty$

- 1.5. The closed loop system is stable for
- (A) k > 1.5

(B) 1 < k < 1.5

(D) 0 < k < 1

(D) no positive value of k


Answer:

32. Let $I = \int_C (2z dx + 2y dy + 2x dz)$ where x, y, z are real, and let C be the straight line segment from point A:(0,2,1) to point B:(4,1,-1). The value of I is _____.

Answer: (-11)



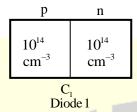33. As shown, two Silicon (Si) abrupt p-n junction diodes are fabricated with uniform donor doping concentration of $N_{D1} = 10^{14} \text{ cm}^{-3}$ and $N_{D2} = 10^{16} \text{ cm}^{-3}$ in the n-regions of the diodes, and uniform acceptor doping concentration of $N_{A1} = 10^{14} \text{ cm}^{-3}$ and $N_{A2} = 10^{16} \text{ cm}^{-3}$ in the p-regions of the diodes, respectively.



p	n
10 ¹⁶ cm ⁻³	10 ¹⁶ cm ⁻³
C Dio	ode 2

Assuming that the reverse bias voltage is >> built-in potentials of the diodes, the ratio C_2/C_1 of their reverse bias capacitances for the same applied reverse bias, is ______.

Answer: (10)

Click here to watch video explanation

34. An optical fiber is kept along the \hat{z} direction. The refractive indices for the electric fields along \hat{x} and \hat{y} directions in the fiber are $n_x = 1.5000$ and $n_y = 1.5001$, respectively $(n_x \neq n_y)$ due to the imperfection in the fiber cross-section). The free space wavelength of a light wave propagating in the fiber is 1.5µm. If the light wave is circularly polarized at the input of the fiber, the minimum propagation distance after which it becomes linearly polarized, in centimeter, is ______.

Answer:

(0.375)

Click here to watch video explanation

35. Two discrete-time signals x[n] and h[n] are both non-zero for n = 0, 1, 2 and are zero otherwise. It is given that

$$x[0]=1, x[1]=2, x[2]=1, h[0]=1.$$

Let y[n] be the linear convolution of x[n] and h[n]. Given that y[1] = 3 and y[2] = 4, the value of the expression (10y[3] + y[4]) is _____.


Answer: (31)



- 36. Which one of the following options correctly describes the locations of the roots of the equation $s^4 + s^2 + 1 = 0$ on the complex plane?
 - (A) Four left half plane (LHP) roots
 - (B) One right half plane (RHP) root, one LHP root and two roots on the imaginary axis
 - (C) Two RHP roots and two LHP roots
 - (D) All four roots are on the imaginary axis

Answer: (C)

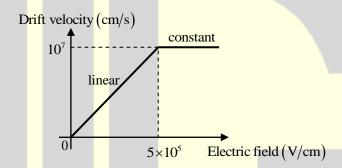37. The dependence of drift velocity of electrons on electric field in a semiconductor is shown below.




The semiconductor has a uniform electron concentration of $n = 1 \times 10^{16} \text{ cm}^{-3}$ and electronic charge $q = 1.6 \times 10^{-19} \text{ C}$. If a bias of 5V is applied across a 1 μm region of this semiconductor, the resulting current density in this region, in kA/cm^2 , is

Answer: (1.6)

Click here to watch video explanation

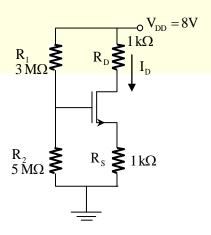38. For the circuit shown, assume that the NMOS transistor is in saturation.





Its threshold voltage V_{tn} =1V and its transconductance parameter $\mu_n C_{ox} \bigg(\frac{W}{L} \bigg)$ =1mA/V². Neglect channel length modulation and body bias effects. Under these conditions, the drain current I_D in mA is


Answer: (2)

Click here to watch video explanation

39. Let X(t) be a wide sense stationary random process with the power spectral density $S_X(f)$ as shown in Figure (a), where f is in Hertz (Hz). The random process X(t) is input to an ideal low pass filter with frequency response

$$\mathbf{H}(\mathbf{f}) = \begin{cases} 1, & |\mathbf{f}| \le \frac{1}{2} \mathbf{Hz} \\ 0, & |\mathbf{f}| > \frac{1}{2} \mathbf{Hz} \end{cases}$$

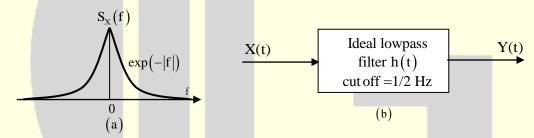As shown in Figure (b). The output of the lowpass filter is Y(t).



Let E be the expectation operator and consider the following statements.

- I. E(X(t)) = E(Y(t))
- II. $E(X^2(t)) = E(Y^2(t))$
- III. $E(Y^2(t))=2$

Select the correct option:

(A) only I is true

(B) only II and III are true

(C) only I and II are true

(D) only I and III are true

Answer: (A)



As shown a uniformly doped Silicon (Si) bar of length L = 0.1 µm with a donor concentration **40.** $N_D = 10^{16} \text{ cm}^{-3}$ is illuminated at x = 0 such that electron and hole pairs are generated at the rate of $G_L = G_{L0} \left(1 - \frac{x}{L} \right), 0 \le x \le L, \text{ where } G_{L0} = 10^{17} \, \text{cm}^{-3} \text{s}^{-1}. \text{ Hole lifetime is } 10^{-4} \, \text{s, electronic charge}$ $q=1.6\times 10^{-19}\,C, \text{hole diffusion coefficient } D_{_p}=100\,\text{cm}^2/\text{s} \text{ and low level injection condition prevails}.$

$$Si \left(N_D = 10^{16} \text{ cm}^{-3}\right)$$

$$x = 0$$

$$L = 0.1 \mu\text{m}$$

Assuming a linearly decaying steady state excess hole concentration that goes to 0 at x = L, the magnitude of the diffusion current density at x = L/2, in A/cm², is _____.

(16) Answer:

Click here to watch video explanation

The Nyquist plot of the transfer function 41.

$$G(s) = \frac{k}{(s^2 + 2s + 2)(s + 2)}$$

does not encircle the point(-1+j0) for k = 10 but does encircle the point(-1+j0) for k = 100.

Then the closed loop system (having unity gain feedback) is


- (A) stable for k = 10 and stable for k = 100
- (B) stable for k = 10 and unstable for k = 100
- (C) unstable for k = 10 and stable for k = 100
- unstable for k = 10 and unstable for k = 100

Answer:

(B)



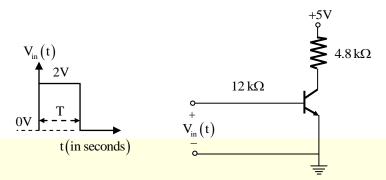42. In the figure shown, the npn transistor acts as a switch



For the input $V_{in}(t)$ as shown in the figure, the transistor switches between the cut-off and saturation regions of operation, when T is large. Assume collector-to-emitter voltage saturation $V_{CE(sat)} = 0.2V$ and base-to-emitter voltage $V_{BE} = 0.7V$. The minimum value of the common-base current gain (α) of the transistor for the switching should be _____.

Answer: (0.9

Click here to watch video explanation

43. A three dimensional region R of finite volume is described by

$$x^2 + y^2 \le z^3; 0 \le z \le 1,$$

Where x, y, z are real. The volume of R (up to two decimal places) is ______.

Answer: (0.79)

Click here to watch video explanation

44. The expression for an electric field in free space is

$$\vec{E} = E_0 \left(\hat{x} + \hat{y} + j2\hat{z} \right) e^{-j(\omega t - kx + ky)}$$

Where x, y, z represent the spatial coordinates, t represents time, and ω , k are constants.


This electric field

- (A) Does not represent a plane wave
- (B) represents a circularly polarized plane wave propagating normal to the z-axis.
- (C) represents an elliptically polarized plane wave propagating along the x-y plane.
- (D) represents a linearly polarized plane wave.

Answer: (C)



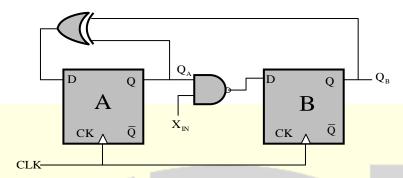45. A finite state machine (FSM) is implemented using the D flip-flops A and B, and logic gates, as shown in the figure below. The four possible states of the FSM are $Q_A Q_B = 00,01,10$ and 11.



Assume that X_{IN} is held at a constant logic level throughout the operation of the FSM. When the FSM is initialized to the state $Q_AQ_B=00$ and clocked, after a few clock cycles, it starts cycling through

- (A) all of the four possible states if $X_{1N} = 1$
- (B) three of the four possible states if $X_{1N} = 0$
- (C) only two of the four possible states if $X_{IN} = 1$
- (D) only two of the four possible states if $X_{1N} = 0$

Answer: (D)

- 46. Let x(t) be a continuous time periodic signal with fundamental period T = 1 seconds. Let $\begin{bmatrix} a_k \end{bmatrix}$ be the complex. Fourier series coefficients of x(t), where k is integer valued. Consider the following statements about x(3t).
 - I. The complex Fourier series coefficient of x(3t) are $[a_k]$ where k is integer valued
 - II. The complex Fourier series coefficient of x(3t) are $[3a_k]$ where k is integer valued
 - **III.** The fundamental angular frequency of x(3t) is 6π rad/s

For the three statements above which one of the following is correct?

(A) only II and III are true


(B) only I and III are true

(C) only III is true

(D) only I is true

Answer: (B)

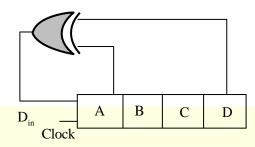47. A 4-bit shift register circuit configured for right-shift operation, i.e, $D_{in} \rightarrow A, A \rightarrow B, B \rightarrow C, C \rightarrow D$, is shown.



If the present state of the shift register is ABCD = 1101, the number of clock cycles required to reach the state ABCD = 1111 is ______.

Answer: (10)

48. Let $f(x) = e^{x+x^2}$ for real x. From among the following, choose the Taylor series approximation of f(x) around x = 0, which includes all powers of x less than or equal to 3.

(A)
$$1 + x + x^2 + x^3$$

(B)
$$1+x+\frac{3}{2}x^2+x^3$$

(C)
$$1+x+\frac{3}{2}x^2+\frac{7}{6}x^3$$

(D)
$$1+x+3x^2+7x^3$$

Answer: (C)

Click here to watch video explanation

49. The following FIVE instructions were executed on an 8085 microprocessor.

MVI A, 33H

MVI B, 78H

ADD B

CMA

ANI 32H

The Accumulator value immediately after the execution of the fifth instruction is


- (A) 00H
- (B) 10H
- (C) 11H
- (D) 32H

Answer: (B)



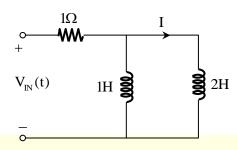50. In the circuit shown, the voltage $V_{IN}(t)$ is described by:

$$V_{IN} = \begin{cases} 0, & \text{for } t < 0 \\ 15 \text{ volts} & \text{for } t \ge 0 \end{cases}$$



Where t is in seconds. The time (in seconds) at which the current I in the circuit will reach the value 2 Amperes is ______.

Answer: (0.34)

Click here to watch video explanation

A half wavelength dipole is kept in the x-y plane and oriented along 45° from the x-axis. Determine the direction of null in the radiation pattern for $0 \le \phi \le \pi$. Here the angle $\theta(0 \le \theta < \pi)$ is measured from the z-axis, and the angle $\phi(0 \le \phi \le 2\pi)$ is measured from the x-axis in the x-y plane.

(A)
$$\theta = 90^{\circ}, \phi = 45^{\circ}$$

(B)
$$\theta = 45^{\circ}, \phi = 90^{\circ}$$


(C)
$$\theta = 90^{\circ}, \phi = 135^{\circ}$$

(D)
$$\theta = 45^{\circ}, \phi = 135^{\circ}$$

Answer: (A)

Click here to watch video explanation

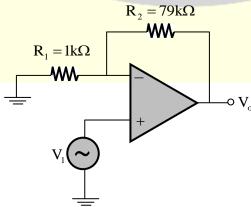52. The amplifier circuit shown in the figure is implemented using a compensated operational amplifier (op-amp), and has an open-loop voltage gain, $A_o = 10^5 \text{ V/V}$ and an open-loop cut-off frequency $f_c = 8\text{Hz}$.





The voltage gain of the amplifier at 15 kHz, in V/V is _____.

Answer: (44.3)

Click here to watch video explanation

53. Let h[n] be the impulse response of a discrete-time linear time invariant (LTI) filter. The impulse response is given by

$$h[0] = \frac{1}{3}; h[1] = \frac{1}{3}; h[2] = \frac{1}{3}; \text{ and } h[n] = 0 \text{ for } n < 0 \text{ and } n > 2.$$

Let $H(\omega)$ be the discrete-time Fourier system transform (DTFT) of h[n], where ω is the normalized angular frequency in radians. Given that $H(\omega_0)=0$ and $0<\omega_0<\pi$, the value of ω_0 (in radians) is equal to ______.

Answer: (2.094)

- 54. Which one of the following gives the simplified sum of products expression for the Boolean function $F = m_0 + m_2 + m_3 + m_5$, where m_0, m_2, m_3 and m_5 are minterms corresponding to the inputs A, B and C with A as the MSB and C as the LSB?
 - (A) $\overline{A}B + \overline{A}\overline{B}\overline{C} + A\overline{B}C$

(B) $\bar{A}\bar{C} + \bar{A}B + A\bar{B}C$

(C) $\bar{A}\bar{C} + A\bar{B} + A\bar{B}C$

(D) $\overline{A}BC + \overline{A}\overline{C} + A\overline{B}C$

Answer: (B)

55. A continuous time signal $x(t) = 4\cos(200\pi t) + 8\cos(400\pi t)$, where t is in seconds, is the input to a linear time invariant (LTI) filter with the impulse response

$$h(t) = \begin{cases} \frac{2\sin(300\pi t)}{\pi t}, & t \neq 0 \\ 600, & t = 0 \end{cases}$$

Let y(t) be the output of this filter. The maximum value of |y(t)| is _____.

Answer: (B)

*** END OF THE PAPER ***